

Exploring Circuits - Task Card

Now that you have successfully created series and parallel circuits, let's see what else you can do.

YOUR TASK

Create your own circuit designs and observe their effectiveness

For each design you create:

- * Sketch the circuit.
- * Describe how effective it was.

Then create another circuit!

Having trouble coming up with ideas?

Try these:

Create a parallel circuit with an additional loop.

Add an additional battery to your circuit.

Try connecting each part of your circuit in different sequences.

Exploring Circuits - Task Card

Now that you have successfully created series and parallel circuits, let's see what else you can do.

YOUR TASK

Create your own circuit designs and observe their effectiveness

For each design you create:

- * Sketch the circuit.
- * Describe how effective it was.

Then create another circuit!

Having trouble coming up with ideas?

Try these:

Create a parallel circuit with an additional loop.

Add an additional battery to your circuit.

Try connecting each part of your circuit in different sequences.